



华南理工大学
South China University of Technology

Intro to Computer Science and Software Engineering

Gates and Circuits

Dr Yubei Lin

yupilin@scut.edu.cn

School of Software Engineering

Computer and computation

A electronic computer is a tool that can carry out the computation we have discussed.

- the processor unit or chip

Binary
(base 2)

One bit addition

A			0			
B	+		0	+		
		0	0			

A						
B	+			+		

carry sum

carry sum

Arithmetic
operations

- **Addition**
- Subtraction
- Multiplication
- division



Computer and computation

A electronic computer is a tool that can carry out the computation we have discussed.

- the processor unit or chip

Binary (base 2)

Arithmetic
operations

- **Addition**
- Subtraction
- Multiplication
- division

One bit addition

A			0
B	+		0
		0	0

			0
+			1
	0		1

A			1
B	+		0
		0	1

			1
+			1
	1		0

carry sum

carry sum



How addition of
Binary system
can be
implemented
by electronic
units?

Computer and computation

A electronic computer is a tool that can carry out all the computation we have discussed.

- the processor unit

Binary
(base 2)

Boolean
algebra

Arithmetic
operations

- **Addition**
- Subtraction
- Multiplication
- division

Operations:
NOT
AND
OR
XOR
NAND
NOR





Computer and computation

A electronic computer is a tool that can carry out all the computation we have discussed.

- the processor unit

Binary
(base 2)

Boolean
algebra

Arithmetic
operations

- **Addition**
- Subtraction
- Multiplication
- division



Operations:
NOT
AND
OR
XOR
NAND
NOR

How addition
of Binary
system can be
implemented
by Boolean
Algebra?

Computer and computation



“A + B” expression, A and B are variables

A + B

A and B are decimal integers in [0,9]

+: addition

A ● B

A and B can be true (1) or false (0)

● : AND

Algebra

A + B

A and B are binaries in [0,1]

+: addition

Boolean algebra

Three different, but equally powerful ways


- Boolean expressions
- Logic diagrams (Gates and Circuits)
- Truth tables

NOT

Boolean Expression

$$X = A'$$

Logic Diagram Symbol

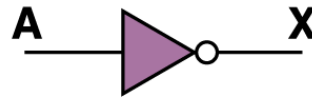

Truth Table


A	X
0	1
1	0

AND

Boolean Expression

$$X = A \cdot B$$

Logic Diagram Symbol

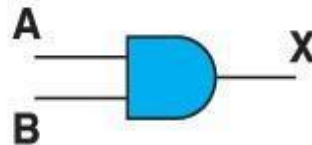

Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Gates




OR

Boolean Expression

$$X = A + B$$

Logic Diagram Symbol

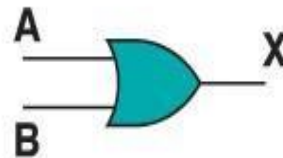

Truth Table


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

XOR

Boolean Expression

$$X = A \oplus B$$

Logic Diagram Symbol

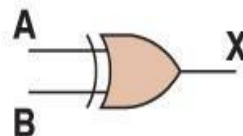

Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Gates




NAND

Boolean Expression

$$X = (A \cdot B)'$$

Logic Diagram Symbol

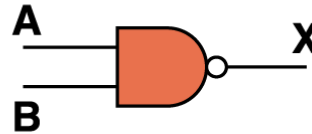

Truth Table


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

NOR

Boolean Expression

$$X = (A + B)'$$

Logic Diagram Symbol

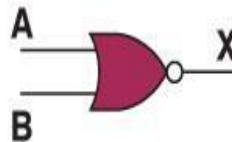

Truth Table

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Boolean algebra




Boolean expression

$$\text{sum} = A \oplus B$$

$$\text{Carry} = A \bullet B$$

Logical diagram

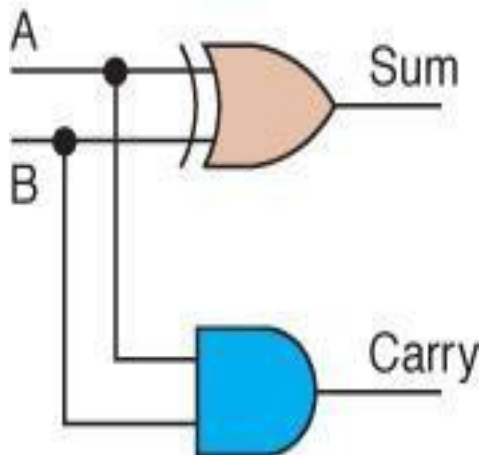

Truth table

		sum	carry
A	B	$A \oplus B$	$A \bullet B$
0	0		
0	1		
1	0		
1	1		

Boolean algebra



Binary (base 2)

One bits addition

		0	A B
+		0	
	0	0	

		0	A B
+		1	
	0	1	

		1	A B
+		0	
	0	1	

		1	A B
+		1	
	1	0	

carry sum

carry sum

Truth table

		sum	carry
A	B	$A \oplus B$	$A \odot B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean algebra



Binary (base 2)

One bits addition

		0	A B
+		0	
	0	0	

		0	A B
+		1	
	0	1	

		1	A B
+		0	
	0	1	


		1	A B
+		1	
	1	0	

carry sum

carry sum

$$\text{sum} = A \oplus B$$


$$\text{Carry} = A \bullet B$$

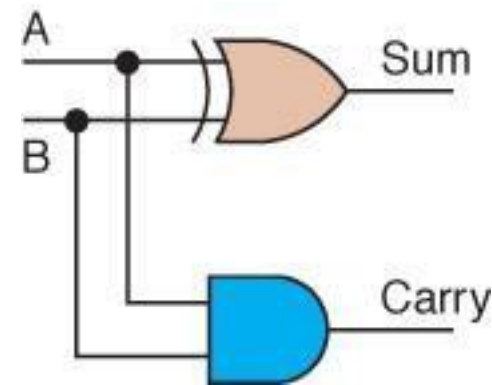

Half Adder
(two gates)

Boolean algebra

Full Adder (five gates)

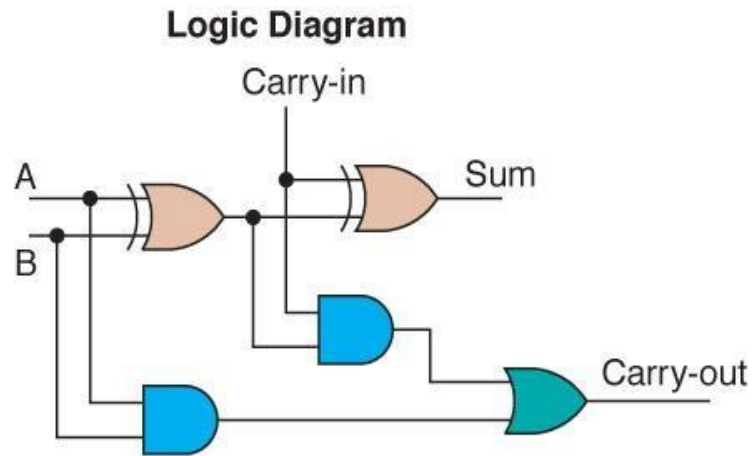


Truth Table

A	B	Carry-in	Sum	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A circuit is a combination of integrated gates.

- More gates for two-bit addition
- Chips (Integrated Circuits) use many gates
 - Very-Large-Scale Integration (VLSI): more than 100, 000

Computer and computation

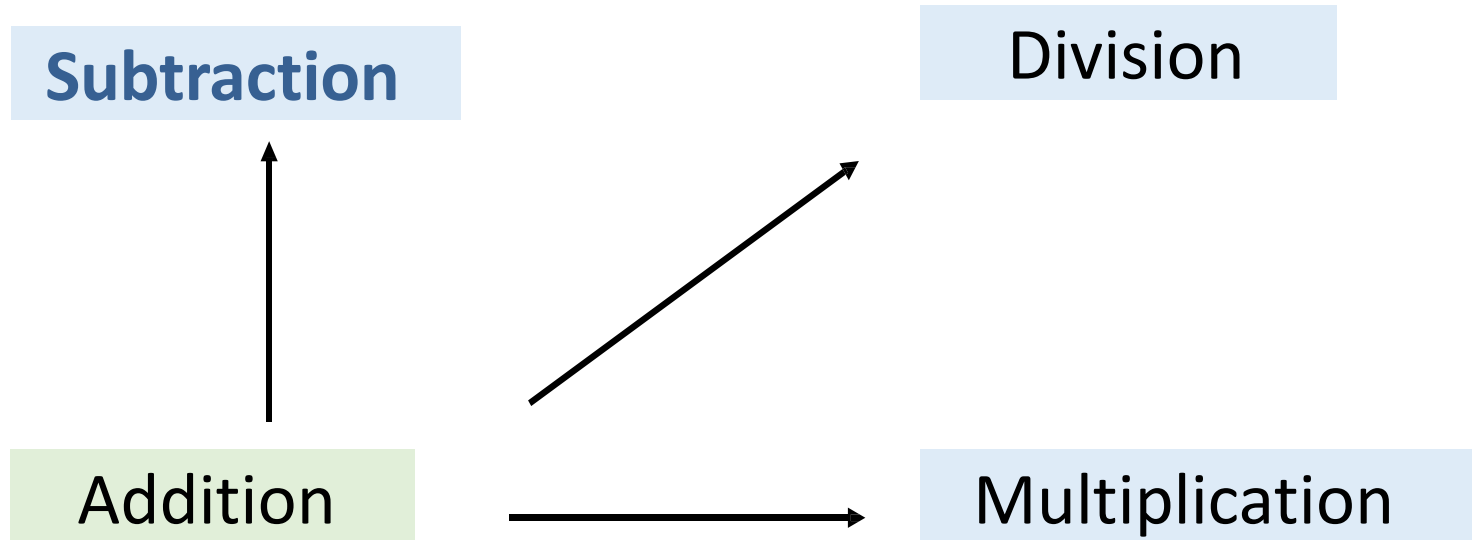

How about a circuit can add two 64-bit binary numbers?

- 64-bit chip

Computer and computation



A electronic computer is a tool that can carry out all the computation we have discussed.

- the processor unit

Binary
(base 2)

Boolean
algebra





Gates and Circuits
using transistors

Arithmetic
operations

- **Addition**
- **Subtraction**
- **Multiplication**
- **division**

Operations:
NOT
AND
OR
XOR
NAND
NOR

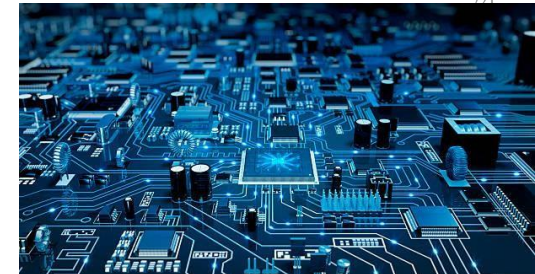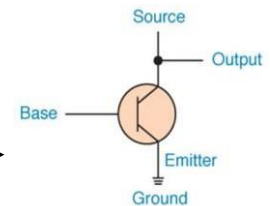

Computer and computation



A electronic computer is a tool that can carry out all the computation we have discussed.

- the processor unit




Binary
(base 2)

Boolean
algebra




Gates and Circuits
using transistors

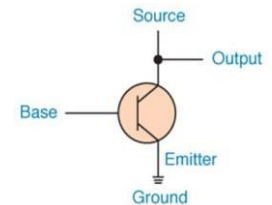How Boolean Algebra can be implemented
by electronic units?




所有图

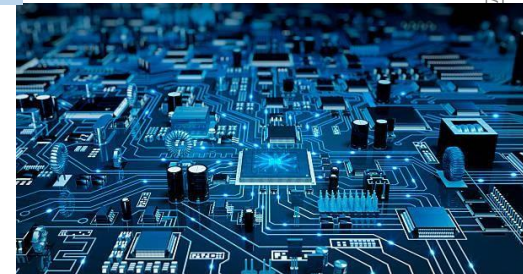

Constructing gates using transistors



High
voltage

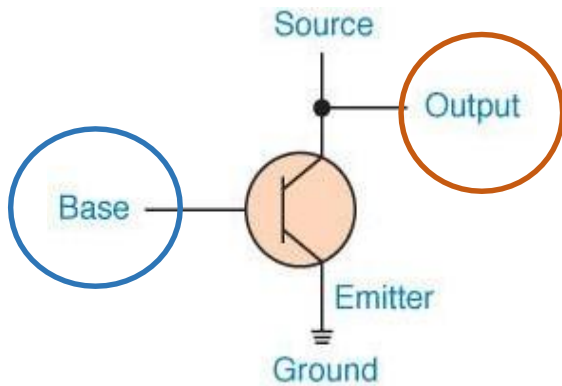


0 voltage

- A transistor has three terminals
 - A source
 - A base (input)
 - An emitter, typically connected to a ground wire


Base	Output
High 1	Low 0
Low 0	High 1

It is made of semiconductor material, usually silicon.

Constructing gates using transistors

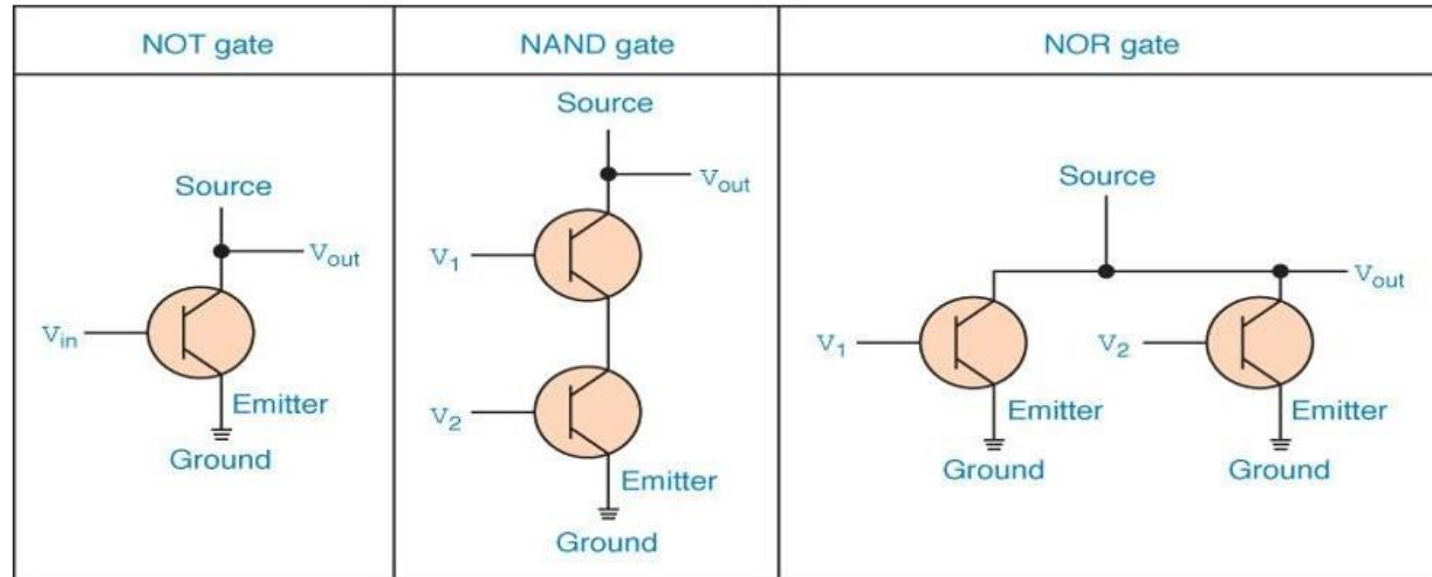

Integrated Circuits (IC)

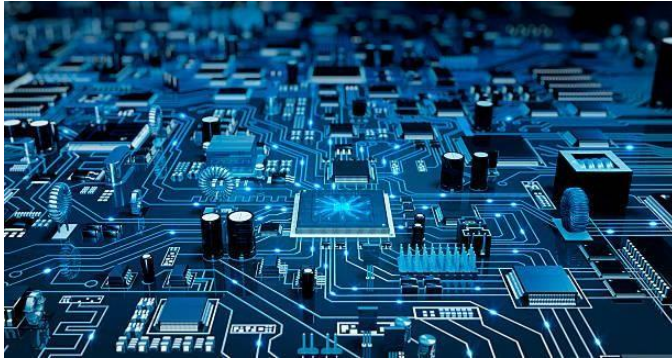

CPU chips



Abbreviation		Name	Number of Gates
SSI		Small-Scale Integration	1 to 10
MSI		Medium-Scale Integration	10 to 100
LSI		Large-Scale Integration	100 to 100,000
VLSI		Very-Large-Scale Integration	more than 100,000

More about transistors



<https://baike.baidu.com/item/%E6%99%B6%E4%B5%A1/569042?fr=aladdin#13>

<https://www.bilibili.com/video/av65427291/>

<https://v.qq.com/x/page/r0360x2dgys.html>